

LMH0034

Application Note 1372 LMH0034 PCB Layout Techniques



Literature Number: SNLA071A

LMH0034 PCB Layout Techniques

National Semiconductor
Application Note 1372
Gary Melchior
July 2006



Introduction

The LMH0034 multi-rate adaptive cable equalizer requires careful attention to PCB layout to achieve optimal performance. It is a high performance analog device and must be treated as such. More specifically, it is a high-gain, wide-band, analog, RF, AGC amplifier-filter. Its successful operation depends on good PCB layout techniques.

Causes and Effects of Common Equalizer Problems

The gain of the LMH0034 equalizer is at a maximum when the input signal is at a minimum. This occurs at maximum cable length as well as when the cable is unconnected (no input signal). Interfering signals and noise can be amplified under these maximum-gain conditions, severely degrading equalizer performance. Even a small amount of noise or interference can cause major performance problems for an adaptive cable equalizer.

Improper PCB layout leads to a number of problems, including:

- Failure to equalize the maximum cable length
- Data errors at long cable lengths
- Random (garbage) data output when no cable is connected
- Positive carrier detection when no cable is connected

These problems are most commonly caused by failing to isolate the LMH0034 from interference, such as:

- Reception of radiated EMI signals originating in the system enclosure or on the PCB
- Power supply or other noise coupling to the inputs through the input network
- Crosstalk between the input network and adjacent circuits
- Coupling between the input and output circuits of the equalizer
- Crosstalk and noise coupling into the Automatic Equalization Control (AEC) circuit

Preventing PCB Problems

Good PCB layout techniques are essential to minimize or eliminate the effects of interference on the LMH0034. These techniques include:

- Isolation of the equalizer inputs and the AEC circuit from high level signals
- Shielding of input and AEC networks from external signal pickup
- Suppression or attenuation of unwanted interference signals

Figure 1 shows a typical schematic for the LMH0034 equalizer. The following PCB layout recommendations will ensure optimal performance of the LMH0034 as well as other high-speed analog devices.

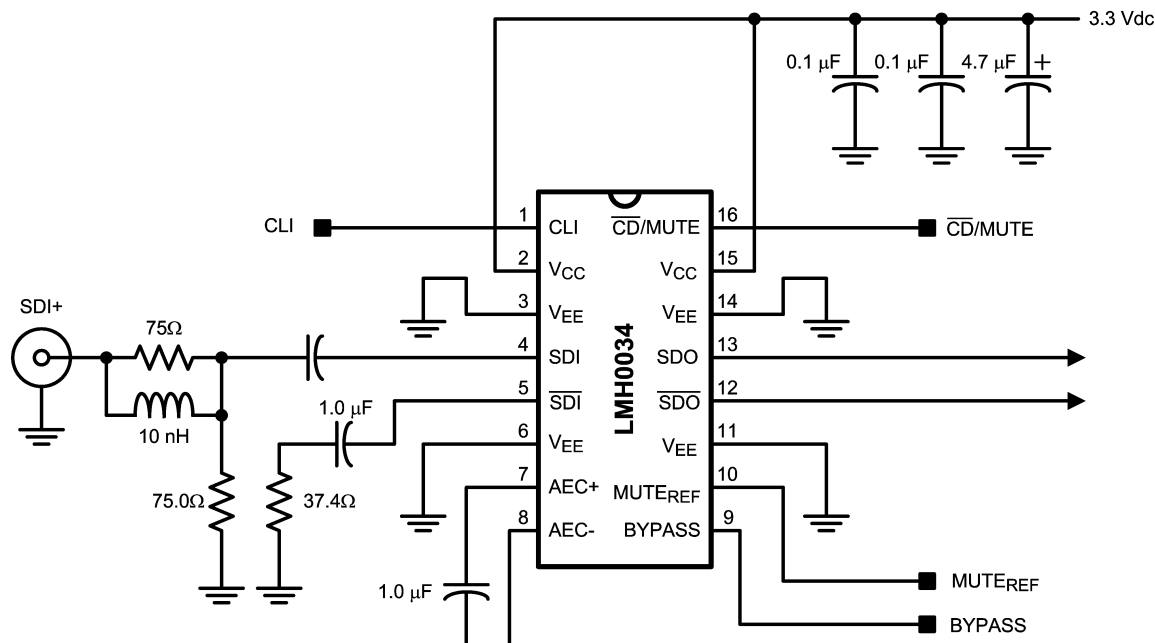


FIGURE 1. Typical LMH0034 Circuit

20143102

Preventing PCB Problems (Continued)

MULTI-LAYER PCB

The LMH0034 requires a multi-layer PCB with separate power and ground layers to achieve the necessary isolation and shielding required for such a high gain and wide bandwidth device. Double-sided PCBs do not offer this and are not appropriate for the LMH0034. A successful LMH0034 PCB design requires a minimum of four layers. Transmission line layers are typically on the top and bottom side (usually microstrip) with separate power and ground planes for the inner layers.

POWER-GROUND SANDWICH

Power and ground layer pairs should be specified with thin dielectrics of 6 mils or less to maximize the intrinsic capacitance of the power-ground "sandwich." This provides very effective high frequency bypassing. Conventional PCB dielectric materials in sandwiches 10 mils (0.25 mm) and less in thickness can be used to achieve intrinsic capacitance of 100 pF/sq. in. (15.7pF/sq. cm.) or more. This "free" capacitance can increase the effective attenuation of the power supply decoupling by 20dB or greater.

DUAL VIAS

Dual vias should be used to minimize inductance in power and ground connections for bypass capacitors, termination resistors, and V_{CC} and V_{EE} pins of the device. They can reduce the interconnect inductance by up to 50%. This reduced inductance extends the effective operating range of bypass capacitors. Also, multiple power or ground pins of the LMH0034 should not be connected to a single via. Each V_{CC} and V_{EE} connection must have its own via (in fact, each connection should have two vias to minimize inductance).

Figure 2 shows an example PCB layout of the LMH0034 equalizer. Note that the bypass capacitors drawn with dashed outlines are intended to be placed on the bottom side of the PCB. This allows the high frequency bypass capacitors to be placed as close as possible to the device power pins without obstructing the layout of the other components. *Figure 2* illustrates several important points about isolating the equalizer from interference.

Preventing PCB Problems (Continued)

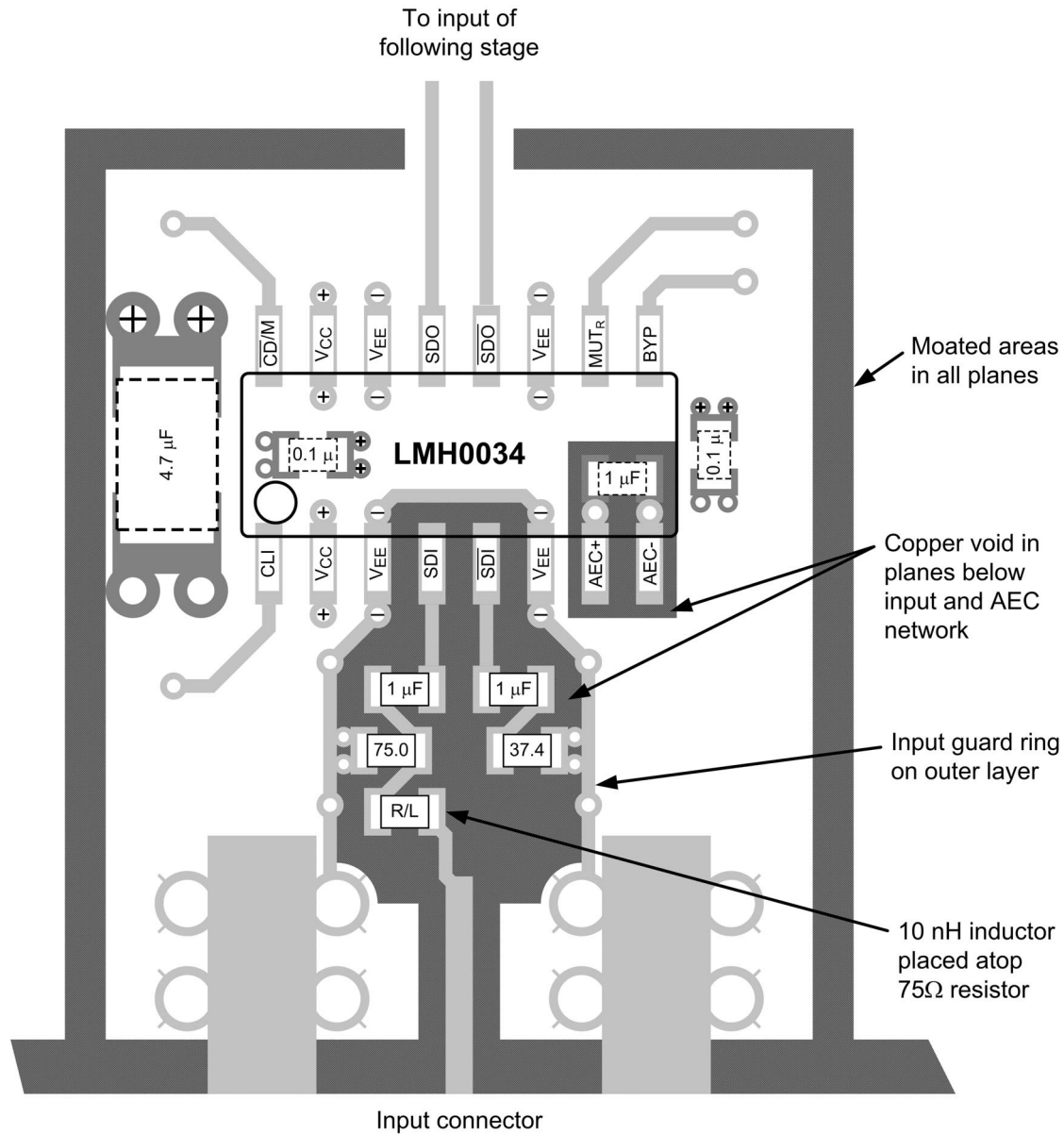


FIGURE 2. LMH0034 Layout with Guard Ring

COPPER VOIDS

Removing, or voiding, the copper in the plane layers below the input network minimizes parasitic capacitance. The dark-shaded area under the input network in *Figure 2* indicates where the planes have been removed. These “voids” minimize the capacitance between the component pads, the component bodies, and the planes. *Figure 2* also shows the copper removed in the plane layers below the AEC network, which prevents power supply noise from coupling into the AEC feedback loop.

MOATS

The LMH0034 is further isolated by removing the copper in all planes in a “moat” surrounding the equalizer. The moat is shown as a dark-shaded rectangle around all circuits in *Figure 2*. Notice that the rectangle is not complete; there is a small opening at the end farthest from the LMH0034 input network to connect the equalizer to the rest of the planes. The moat prevents unwanted currents from adversely affect-

Preventing PCB Problems (Continued)

ing the equalizer. Stray signals from adjacent circuits have a long way to travel to reach the LMH0034 inputs, so they are effectively attenuated.

It is also important to isolate the LMH0034 inputs from its own outputs, or from the output of any nearby cable drivers or other high-level signals. The typical equalizer input tends to be a weak signal (hence the need for equalization) and larger signals can couple into the input signal and corrupt the data.

GUARD RINGS

A grounded guard ring around the input of the equalizer isolates and protects the LMH0034 even more. This is shown in *Figure 2* as a light-shaded ring surrounding the dark-shaded copper void of the input network. The guard ring is grounded by vias in several locations. It should completely enclose the input network.


COMMON MODE REJECTION

The input networks should be symmetrical to take advantage of common mode rejection. Noise and interference picked up by the equalizer input is usually common to both inputs. This noise will be rejected by the differential input of the LMH0034. The layout should be as symmetrical as possible with balanced termination impedances as shown.

COPPER FLOODS

Copper floods can be used on the outer PCB layers in place of the guard ring for additional isolation and shielding, as shown in *Figure 3*. The techniques explained previously apply to PCBs with copper floods as well. Dashed outlines indicate areas where copper should be removed under the input components and AEC circuit, as well as the location of the surrounding moat. The copper flood should be connected to the ground layers at 1 cm intervals to be effective.

Preventing PCB Problems (Continued)

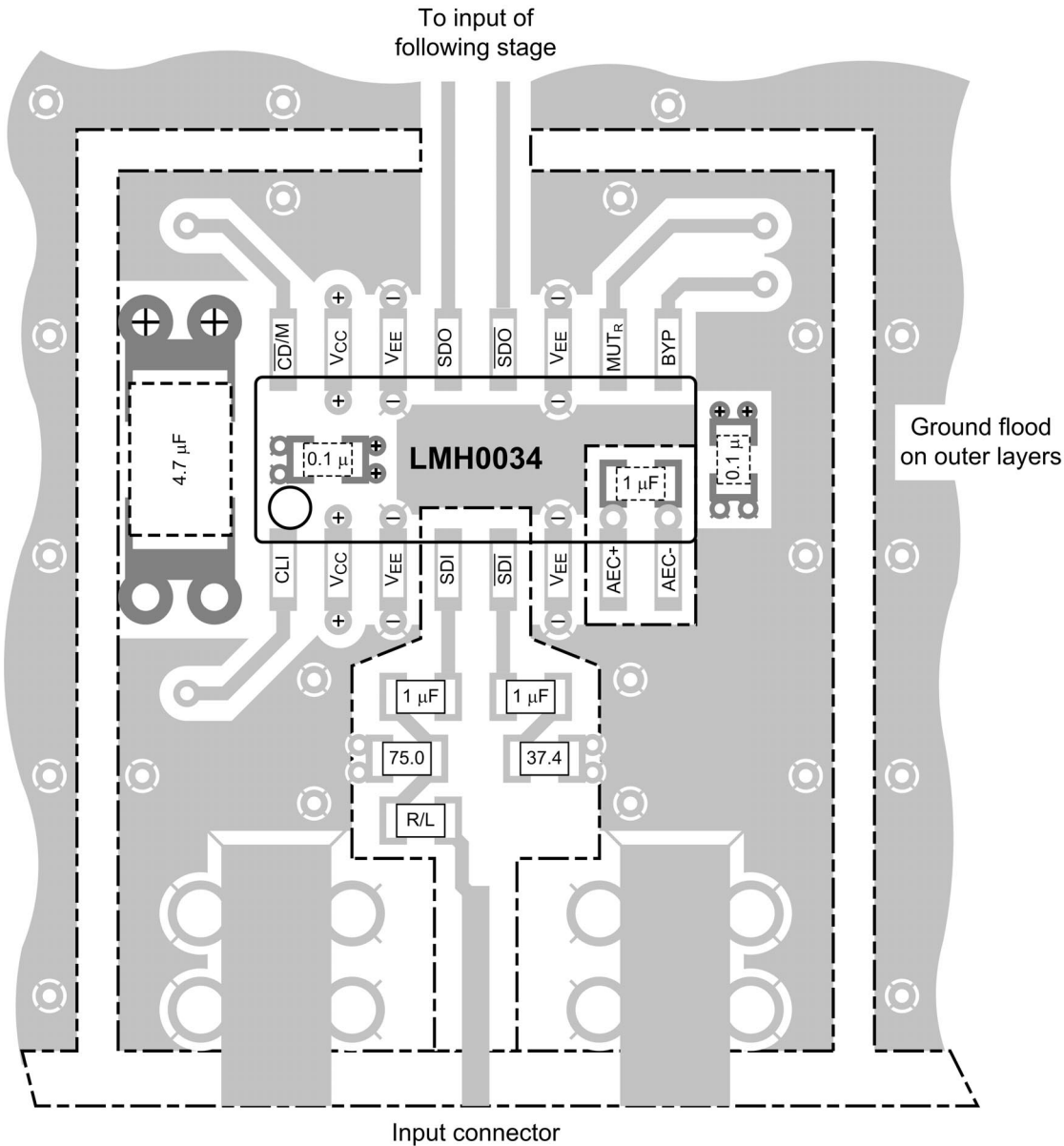

20143104

FIGURE 3. LMH0034 Layout with Copper Floods

ADDITIONAL TECHNIQUES

In addition to reducing or eliminating the effect of interference on the LMH0034, it is important to minimize impedance variations that may cause reflections or otherwise degrade equalizer performance. Additional PCB layout techniques that control impedance and produce a clean PCB layout can improve overall LMH0034 performance.

The BNC input connector shown in the layout diagrams is an in-line surface mount “launcher,” as opposed to a right angle or vertical BNC. This is necessary for tight impedance control in order to meet the return loss requirement of SMPTE 292M and 259M. Right angle BNC connectors are not suitable for controlled impedance situations due to the length of the exposed center pin and ground pins.

Impedance changes can be reduced by routing traces diagonally to the corners of component pads where possible. Rounded corners may be used to further minimize impedance changes caused by the change in PCB trace width. 90-degree corners should never be used with high speed circuits.

The LMH0034 should be placed close to the BNC connector, with the input components as close to the equalizer as possible. Shorter input networks are almost always less troublesome than longer networks. The input network to the LMH0034 should contain no stubs whatsoever. Also note that any termination resistors for the LMH0034 output should be located at the input of the following stage.

Summary

Following these PCB layout techniques will result in improved LMH0034 performance. In summary:

- Use multi-layer PCBs with an effective power-ground sandwich for isolation, shielding, and improved bypassing.
- Use dual vias to minimize inductance in power and ground connections (at least one via per V_{CC} and V_{EE} connection).
- Make use of copper voids to reduce parasitic capacitance and noise.

- Use moats and guard rings for isolation.
- Isolate the LMH0034 inputs from high level signals.
- Take advantage of the common mode rejection offered by differential inputs by using a symmetrical layout.
- Use copper floods for additional shielding and isolation.
- Minimize impedance mismatches.

For a negligible amount of added costs, these techniques will result in less troublesome and all around better performing LMH0034 PCB designs.

National does not assume any responsibility for use of any circuitry described, no circuit patent licenses are implied and National reserves the right at any time without notice to change said circuitry and specifications.

For the most current product information visit us at www.national.com.

LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, and whose failure to perform when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.
2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.

BANNED SUBSTANCE COMPLIANCE

National Semiconductor follows the provisions of the Product Stewardship Guide for Customers (CSP-9-111C2) and Banned Substances and Materials of Interest Specification (CSP-9-111S2) for regulatory environmental compliance. Details may be found at: www.national.com/quality/green.

Lead free products are RoHS compliant.



National Semiconductor
Americas Customer
Support Center
Email: new.feedback@nsc.com
Tel: 1-800-272-9959

www.national.com

National Semiconductor
Europe Customer Support Center
Fax: +49 (0) 180-530 85 86
Email: europa.support@nsc.com
Deutsch Tel: +49 (0) 69 9508 6208
English Tel: +44 (0) 870 24 0 2171
Français Tel: +33 (0) 1 41 91 8790

National Semiconductor
Asia Pacific Customer
Support Center
Email: ap.support@nsc.com

National Semiconductor
Japan Customer Support Center
Fax: 81-3-5639-7507
Email: jpn.feedback@nsc.com
Tel: 81-3-5639-7560

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Audio	www.ti.com/audio
Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DLP® Products	www.dlp.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
OMAP Mobile Processors	www.ti.com/omap
Wireless Connectivity	www.ti.com/wirelessconnectivity

Applications

Communications and Telecom	www.ti.com/communications
Computers and Peripherals	www.ti.com/computers
Consumer Electronics	www.ti.com/consumer-apps
Energy and Lighting	www.ti.com/energy
Industrial	www.ti.com/industrial
Medical	www.ti.com/medical
Security	www.ti.com/security
Space, Avionics and Defense	www.ti.com/space-avionics-defense
Transportation and Automotive	www.ti.com/automotive
Video and Imaging	www.ti.com/video

TI E2E Community Home Page

e2e.ti.com

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2011, Texas Instruments Incorporated